

CSE 210  
Computer Architecture Sessional  
Assignment 3: MIPS Design and  
Simulation

6 December 2024

Group: 02  
Section: A1

Members of the group:

- 2105007 - Nafis Nahian
- 2105008 - Sk. Ashrafuzzaman Nafees
- 2105009 - Abrar Zahin Raihan

# 1 Introduction

A processor, also known as a processing unit, is a digital circuit that carries out operations on data from external sources, such as memory or data streams. While the term "processor" can refer to various types of processing units, it is most commonly associated with the Central Processing Unit (CPU) of a system. The CPU serves as the core of a computer, executing instructions from programs and performing essential computational tasks.

The CPU is composed of intricate electronic circuitry designed to handle fundamental operations, including arithmetic calculations, logical decision-making, control processes, and input/output (I/O) operations. These tasks are executed based on the instructions defined in the computer program, making the CPU central to the functionality of the system.

Among the CPU's primary components is the Arithmetic Logic Unit (ALU), which is responsible for performing mathematical computations and logical comparisons. Additionally, processor registers play a crucial role by providing data to the ALU for processing and storing the results of these operations. Complementing these components is the control unit, which orchestrates the entire process by fetching instructions from memory, interpreting them, and coordinating the activities of the ALU, registers, and other parts of the CPU. This coordinated process ensures that instructions are executed in the correct sequence and timing, maintaining the logical flow of operations within the system.

There are many types of processor design implementation. MIPS (Microprocessor without Interlocked Pipelined Stages) is a reduced instruction set computer (RISC) instruction set architecture (ISA). The Processor Design implementing MIPS ISA is called MIPS processor.

The processor components that we implemented are as follows:

1. **Program Counter and Instruction Memory:** The program counter (PC) is an 8-bit register which activates at the falling edge of the clock signal. After every clock cycle, it adds 1 to its previous address. The value it stores is used as the Instruction Memory address.
2. **Register File:** The Register File is a bank of seven registers. These are denoted as \$zero, \$t0, \$t1, \$t2, \$t3, \$t4, \$t5, and \$sp. The \$sp register acts as the stack pointer, while the \$zero register always holds the value zero. The other registers serve as general-purpose registers.
3. **ALU:** The ALU performs all calculations. It is controlled by a 3-bit ALUop code that determines the type of calculation it performs. It operates on two 8-bit binary numbers.
4. **Control Unit:** The Control Unit decodes the instruction by providing selection inputs to all multiplexers, the Register File, the Data Memory, and the ALU.
5. **Data Memory:** The Data Memory stores stack values and functions as the main memory. It stores data as 8-bit values.

Instruction pipelining is a method used to enhance the efficiency of instruction execution in a processor by dividing the process into distinct stages. Each stage performs a part of the instruction cycle, allowing multiple instructions to overlap in execution. This increases the overall instruction throughput, enabling the processor to execute several instructions simultaneously without reducing the time required to complete an individual instruction.

Generally, each instruction is divided into five stages:

1. Instruction Fetch (IF)
2. Instruction Decode (ID)
3. Execution and Address Calculation (EX)
4. Data Memory Access (MEM)
5. Write Back (WB)

There are situations in pipelining when the next instruction cannot execute in the following clock cycle. These events are called hazards. Hazards are categorized into three types:

1. **Data Hazards:** Occur when an instruction depends on the result of a previous instruction that has not yet completed its execution.
2. **Control Hazards:** Arise when the pipeline is unable to predict the flow of control, typically caused by branch instructions.
3. **Structural Hazards:** Happen when multiple instructions require the same hardware resource simultaneously, leading to resource contention.

The processor we designed supports pipelined datapath for a subset of MIPS instruction set. We considered EX hazard, MEM hazard, load use, load store and double data hazard. We also considered Control/branch hazard, and data hazard during the branching.

## 2 Instruction Set

### 2.1 Instruction Set With Instruction ID

Instruction ID	Category	Type	Instruction
A	Arithmetic	R	add
B	Arithmetic	I	addi
C	Arithmetic	R	sub
D	Arithmetic	I	subi
E	Logic	R	and
F	Logic	I	andi
G	Logic	R	or
H	Logic	I	ori
I	Logic	R	sll
J	Logic	R	srl
K	Logic	R	nor
L	Memory	I	sw
M	Memory	I	lw
N	Control	I	beq
O	Control	I	bneq
P	Control	J	j

### 2.2 Instruction Set With Op-Code

Op-Code	Category	Type	Instruction
0000	Arithmetic	I	subi
0001	Control	I	bneq
0010	Memory	I	sw
0011	Control	I	beq
0100	Arithmetic	R	add
0101	Logic	I	ori
0110	Logic	R	srl
0111	Memory	I	lw
1000	Control	J	j
1001	Logic	R	or
1010	Logic	R	nor
1011	Logic	I	andi
1100	Arithmetic	R	sub
1101	Logic	R	and
1110	Arithmetic	I	addi
1111	Logic	R	sll

### 3 Complete Circuit Diagram

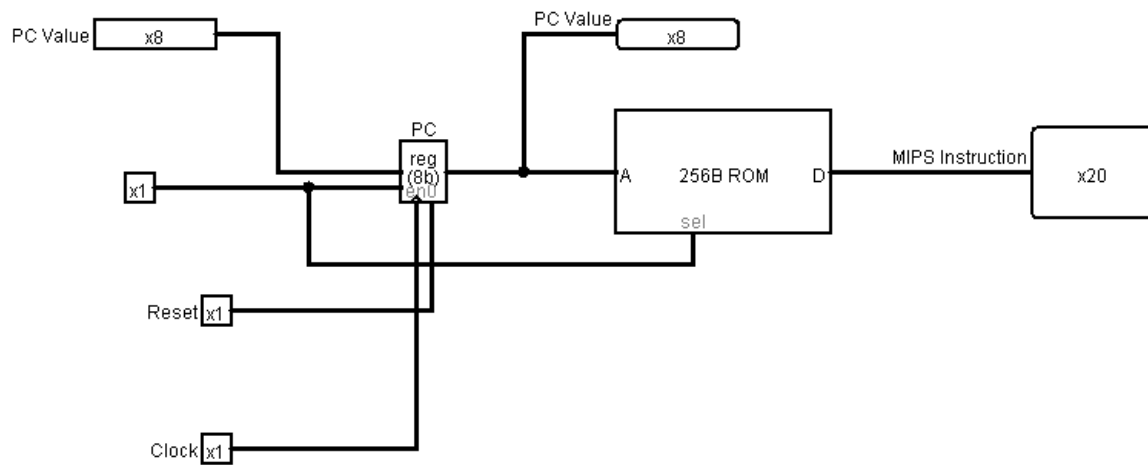


Figure 1: Instruction Memory with Program Counter

 


Figure 2: Data memory with stack

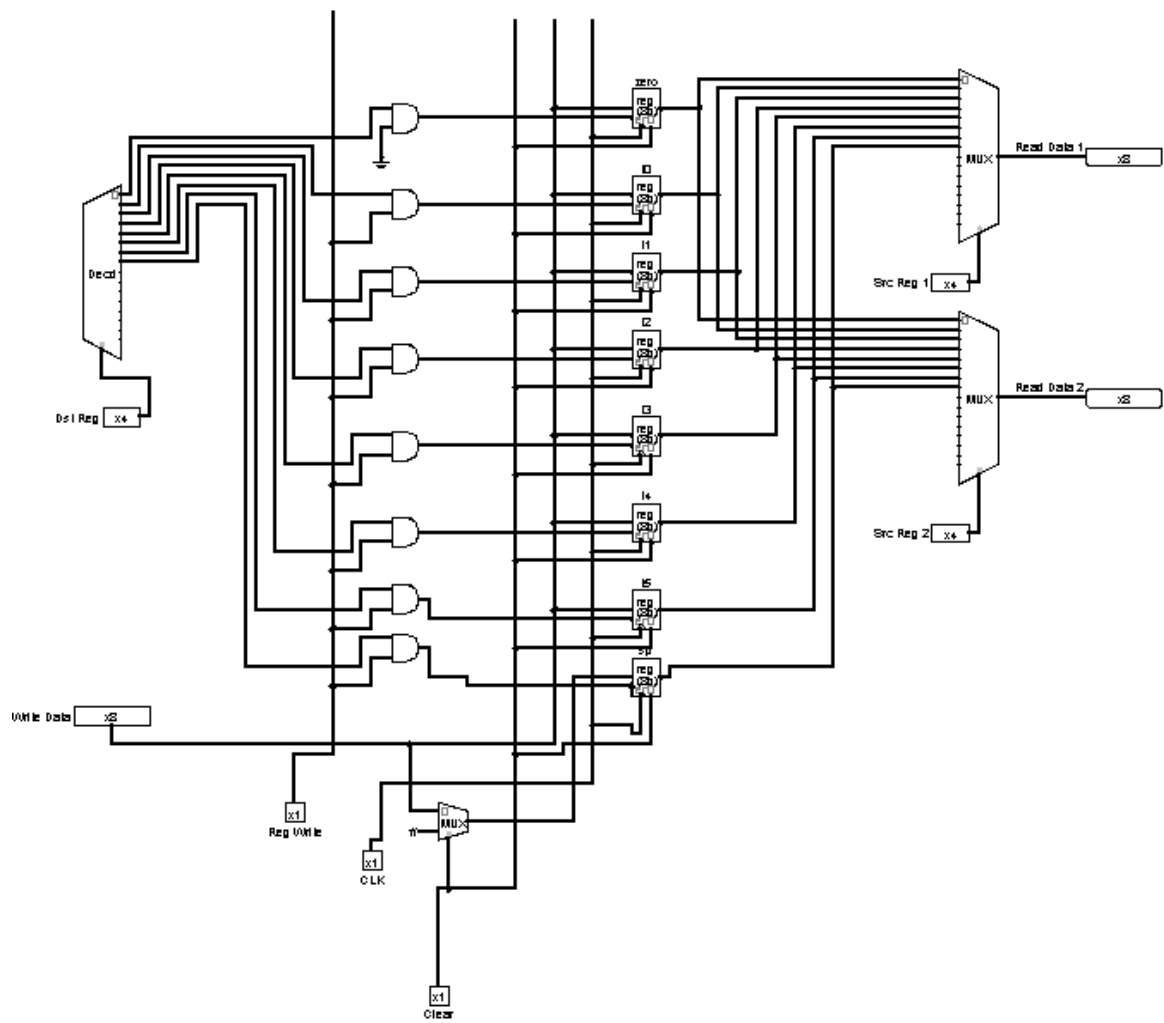


Figure 3: Register Files

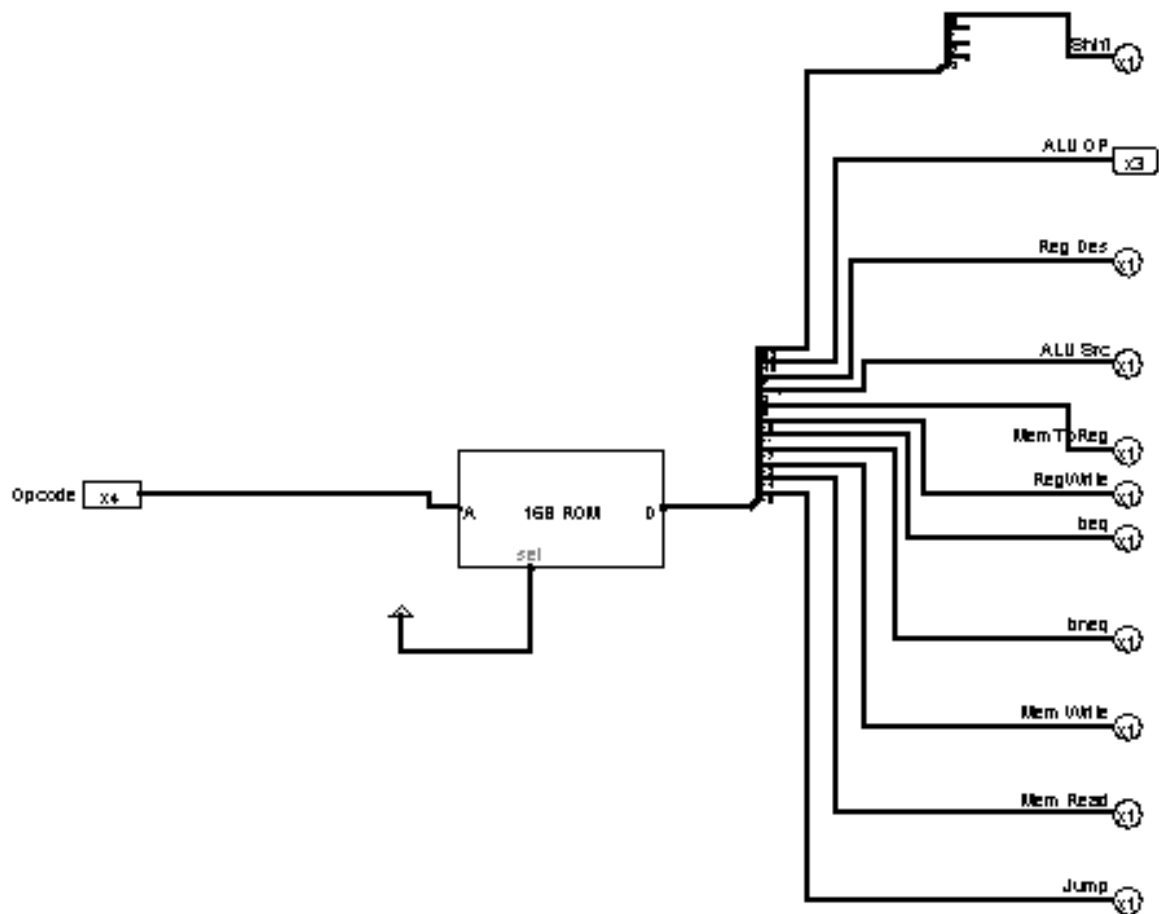


Figure 4: Control Unit

 


Figure 5: Instruction Splitter

 


Figure 6: Stack Logic



 


Figure 7: IF/ID Register

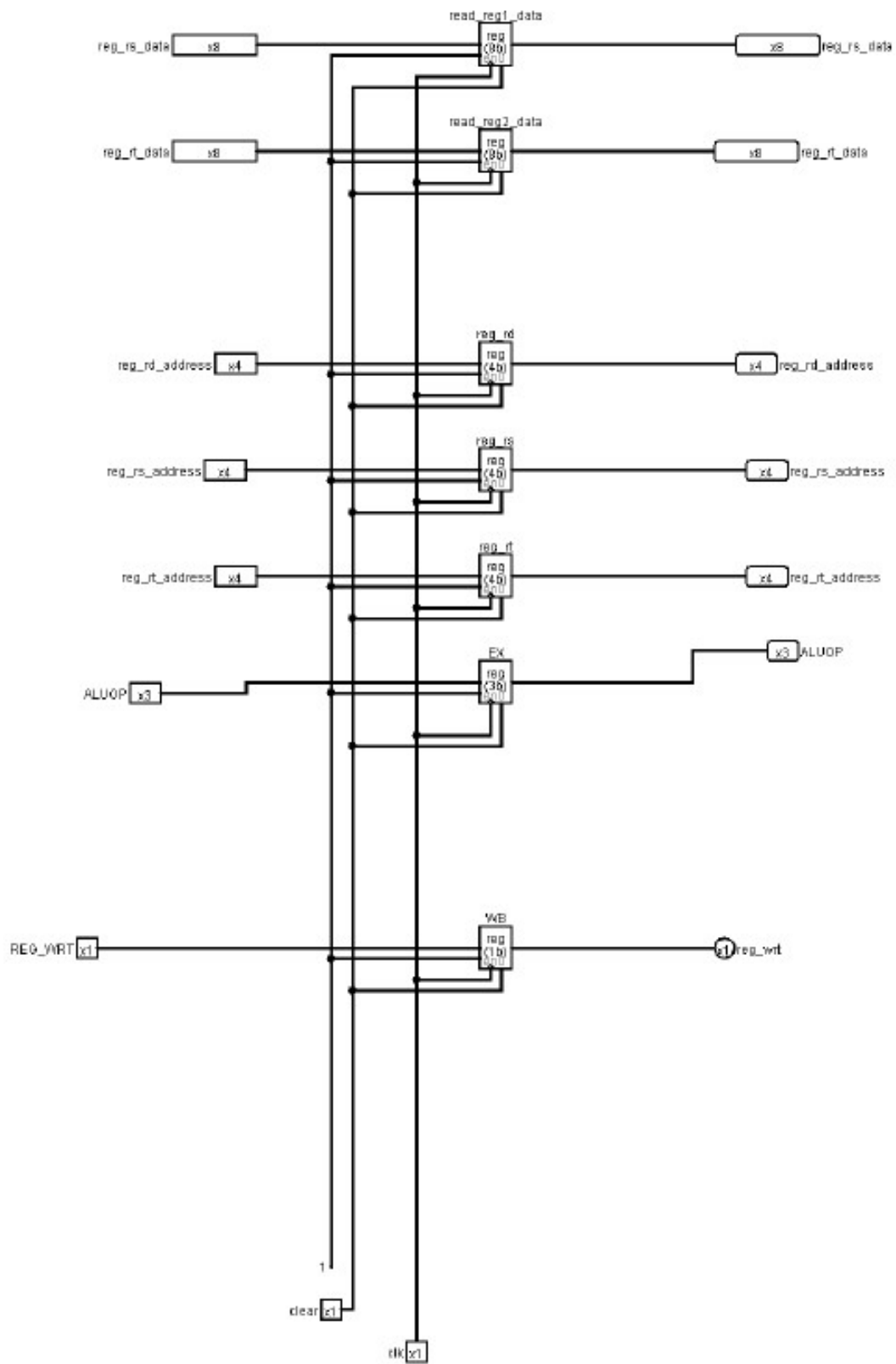


Figure 8: ID/EX Register

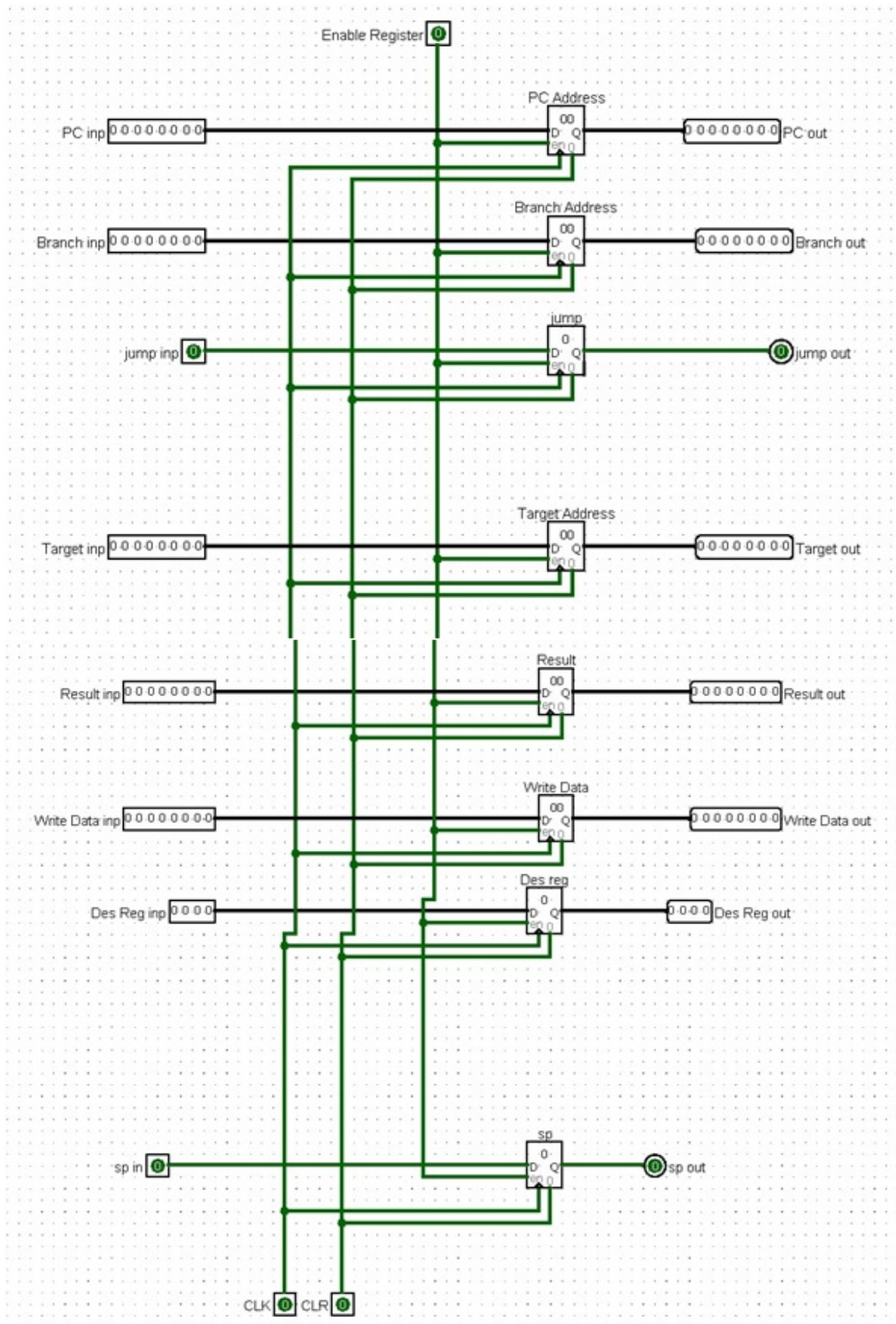


Figure 9: EX/MEM Register

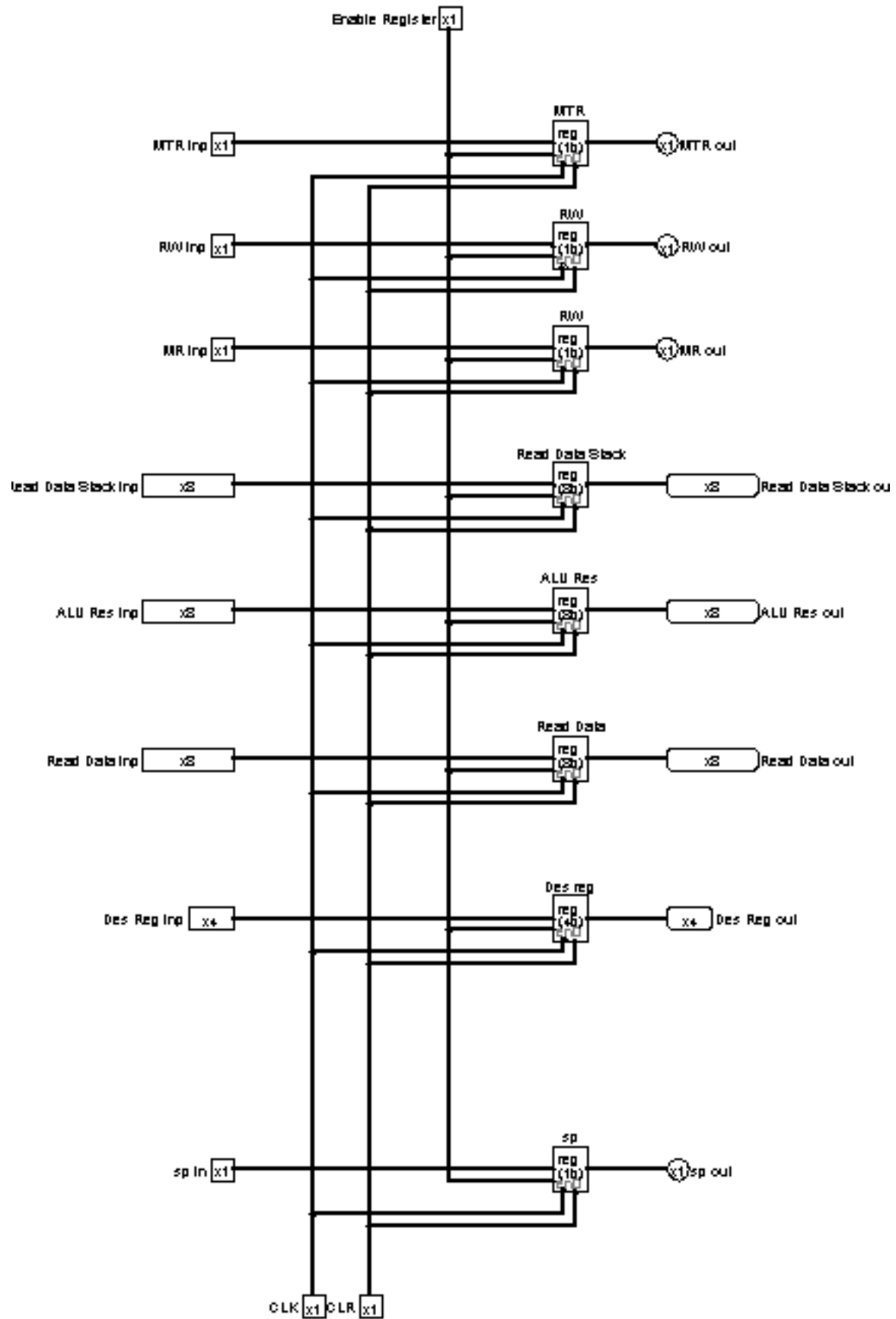


Figure 10: MEM/WB Register

 


Figure 11: Forwarding Unit

 


Figure 12: Load Use Hazard Detector



The diagram illustrates the internal architecture of a MIPS processor, divided into two main stages: Instruction Fetch (IF) and Instruction Decode (ID).


**IF Stage (Instruction Fetch):**

- PC Logic:** The Program Counter (PC) is updated based on the current PC value, a branch prediction (Next Inst), and a branch target (PC+4 Inst). The update logic is shown as a multiplexer (MUX) and an adder.
- Instruction Memory:** The PC value is used to address the Instruction Memory, which outputs the MIPS instruction.
- Reset Logic:** The processor can be reset by either the main reset signal or the instruction memory output.
- Control Signals:** The IF stage is controlled by the CLK (clock) and CLK\_X1 (clock enable) signals.

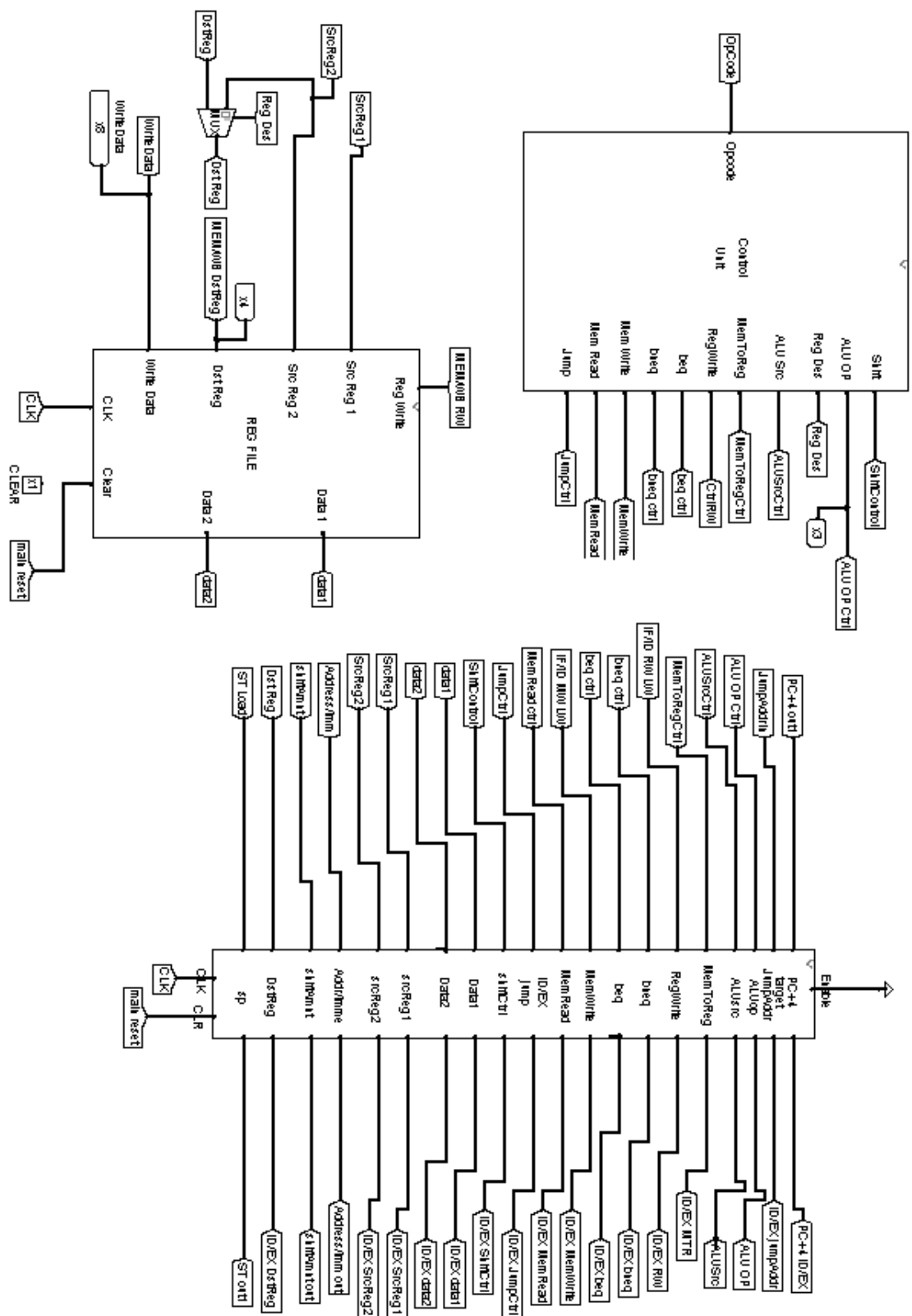
**ID Stage (Instruction Decode):**

- Instruction Register:** The MIPS instruction is stored in the MIPS Inst register.
- Register File:** The instruction is decoded to extract the source register 1 (Src Reg 1), source register 2 (Src Reg 2), target register (Tgt Reg), and the opcode. These are connected to the Register File, which also provides the address and target address for the next stage.
- Control Signals:** The ID stage is controlled by the CLK (clock) and CLK\_X1 (clock enable) signals.

The diagram is labeled with "IF" and "ID" at the bottom, indicating the stages of the processor.





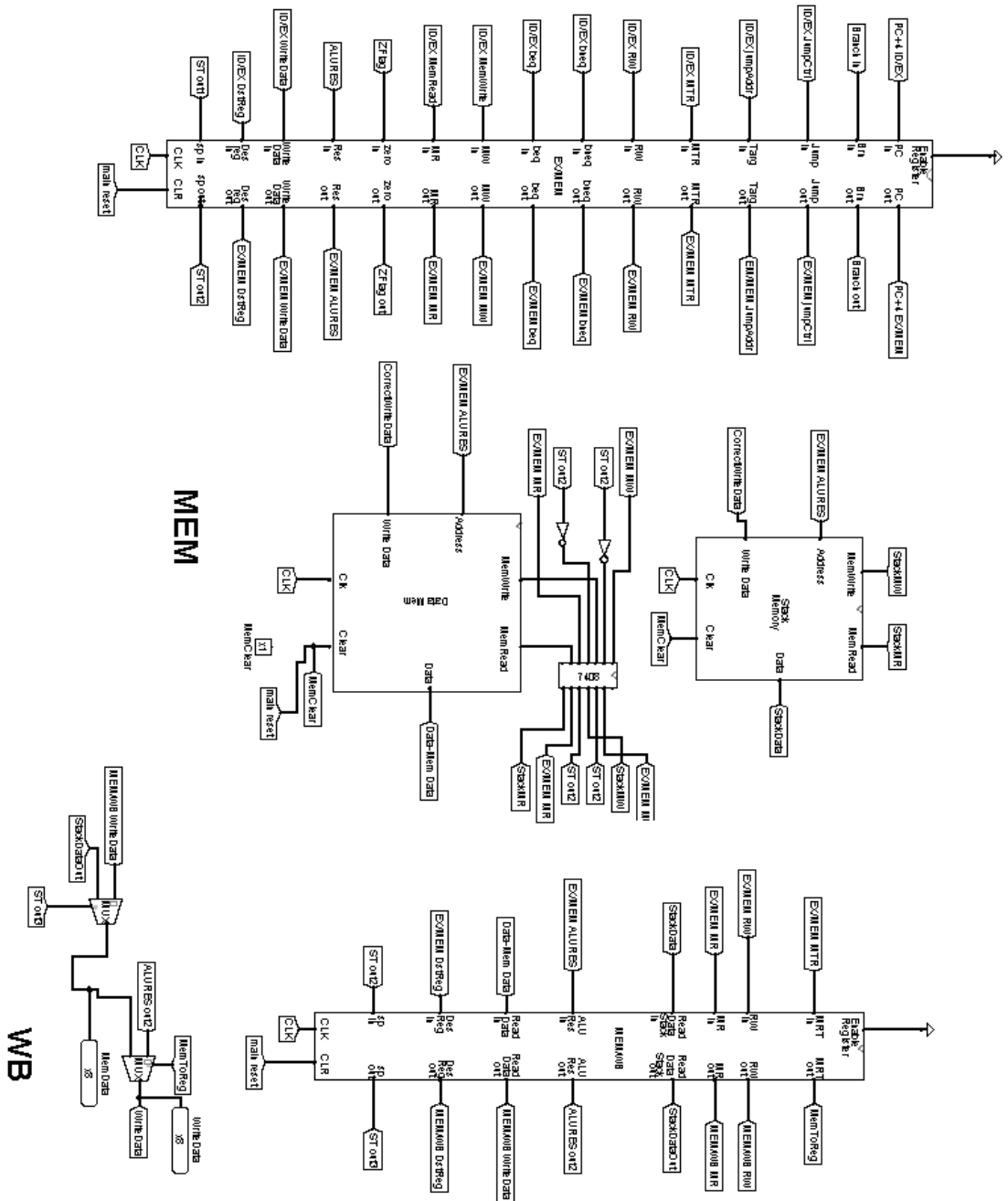



## 4 How to Write and Execute A Program

Write the assembly code without any empty lines in a text file named `in.txt`. Then, run the `assembler.cpp` code to generate `instructions.hex`. This file will be loaded into the instruction memory. Afterward, providing a clock signal will execute the program.

## 5 ICs used with their count

Gate	Gate Count	IC	IC Count
MUX(2-to-1)	8	74157	2
MUX(4-to-1)	3	74153	2
MUX(8-to-1)	2	74151	1
MUX(16-to-1)	2	74150	2
Adder(8-bit)	3	7483	6
Decoder(4-to-16)	1	74154	1
AND(2-bit)	10	7408	3
AND(8-bit)	1	7430	1
OR(2-bit)	4	7432	1
OR(8-bit)	1	7432	1
NOT(1-bit)	1	7404	1
Priority Encoder(2-bit)	1	Priority Encoder(2-bit)	1
Register(8-bit)	33	Register(8-bit)	33
ROM(256X20)	1	ROM(256X20)	1
ROM(256X8)	1	ROM(256X8)	1
ROM(16X13)	1	ROM(16X13)	1
Subtractor(8-bit)	1	Subtractor(8-bit)	1
Comparator(8-bit)	8	Comparator(8-bit)	8
RAM(256X8)	1	RAM(256X8)	1
Clock	1	Clock	1

## 6 Contribution

**Instruction Memory:** 2105009

**Register File:** 2105007, 2105009

**Control Unit:** 2105008, 2105009

**Data Memory:** 2105007, 2105008

**IF/ID, ID/EX:** 2105007, 2105009

**EX/MEM, MEM/WB:** 2105007, 2105008

**Load-use, Load-store, Branch-hazard detector:** 2105007

**Main circuit:** 2105007, 2105008, 2105009

**Report:** 2105007

## 7 Discussion

In the process of designing and implementing the system, we took several careful measures to ensure correctness, efficiency, and ease of debugging. One critical aspect was creating the table for control bits with precision, as any inaccuracies in this table could lead to unexpected outputs. To streamline the design process and minimize wiring errors, we utilized tunnels instead of physical wiring, which not only reduced clutter but also made debugging significantly easier.

Before implementing the circuit, we prepared a hand-drawn diagram to avoid potential faulty connections. This step helped us identify and resolve design flaws early. Additionally, we ensured that the instruction hex file was formatted correctly to prevent errors when loading MIPS instructions into the ROM.

To manage complexity and enhance implementation, we modularized each circuit component into separate `.circ` files. This modular approach facilitated independent testing and debugging of individual components. Moreover, we optimized the circuit by removing unnecessary components and reducing register usage, resulting in a more efficient design.

Finally, we invested considerable time in carefully cross-checking corner cases for each sample test case. This thorough verification process ensured the system's reliability and robustness under various scenarios.